
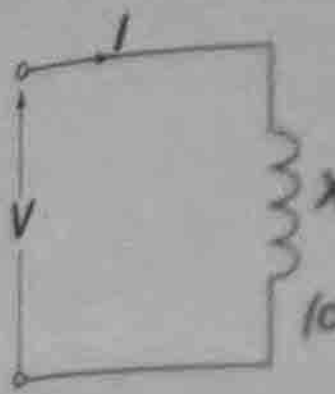




$$V=RI$$

(circuito puramente ohmico)

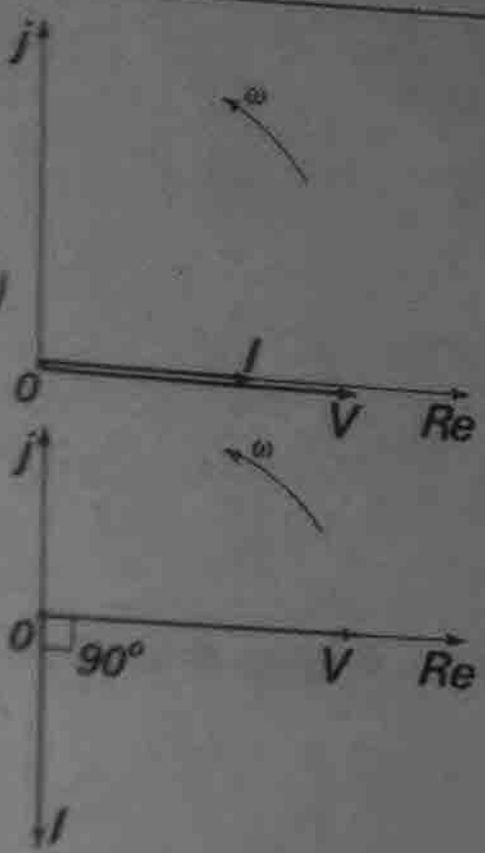



$$V=jX_L I$$

(circuito puramente induttivo)

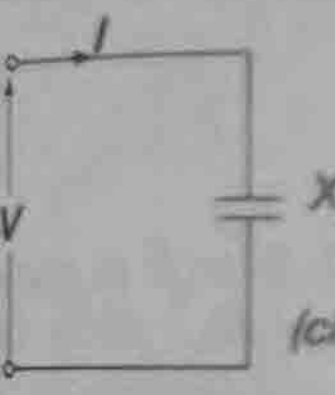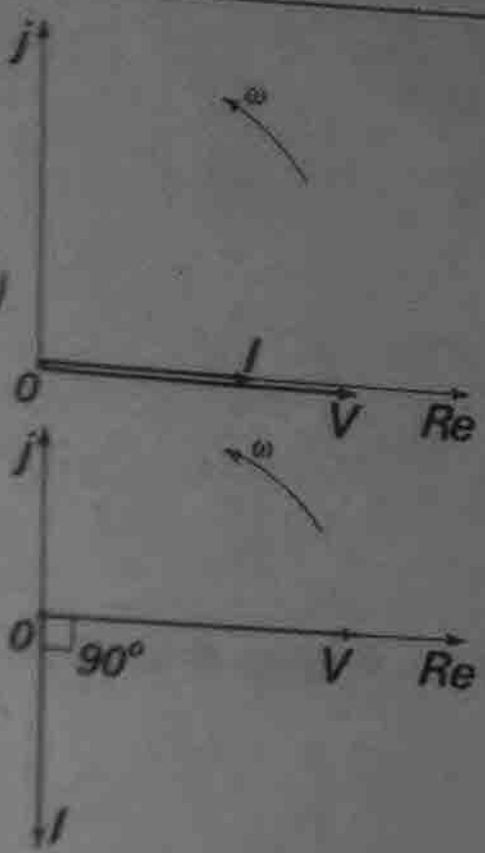

$$V=-jX_C I$$

(circuito puramente capacitivo)

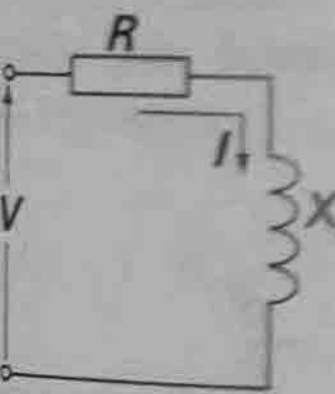
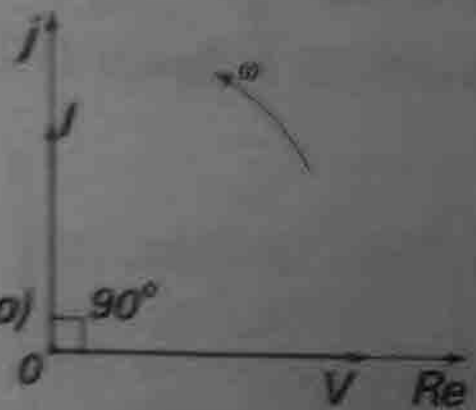


$$Z=R+jX_L$$

$$V=(R+jX_L)I$$

$$\operatorname{tg}\varphi=\frac{X_L}{R}$$

(circuito ohmico-induttivo)

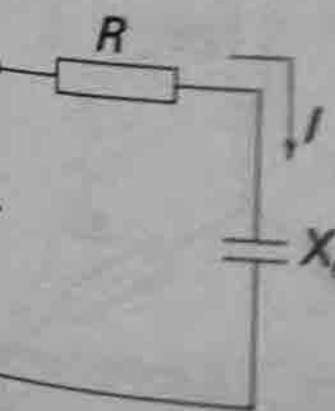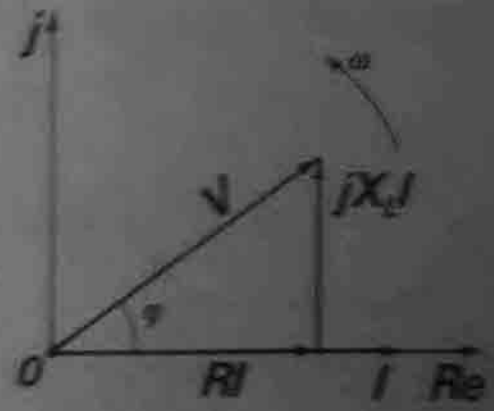


$$Z=R-jX_C$$

$$V=-jX_C I$$

$$\operatorname{tg}\varphi=-\frac{X_C}{R}$$

(circuito ohmico-capacitivo)

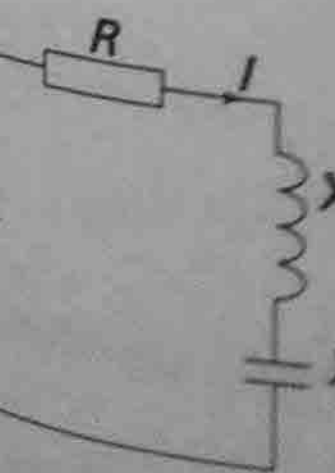


$$Z=R+j(X_L-X_C)$$

$$V=[R+j(X_L-X_C)]I$$

$$\operatorname{tg}\varphi=\frac{X_L-X_C}{R}$$

(circuito R-L-C generico)

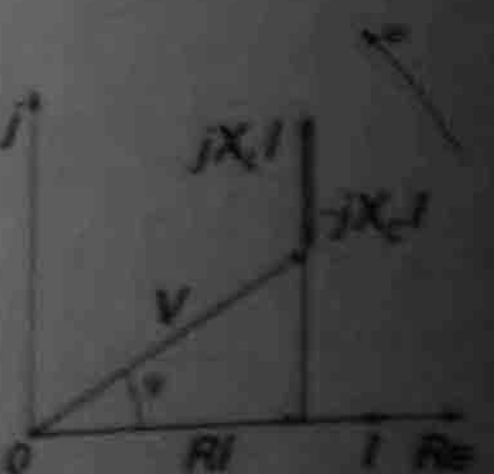

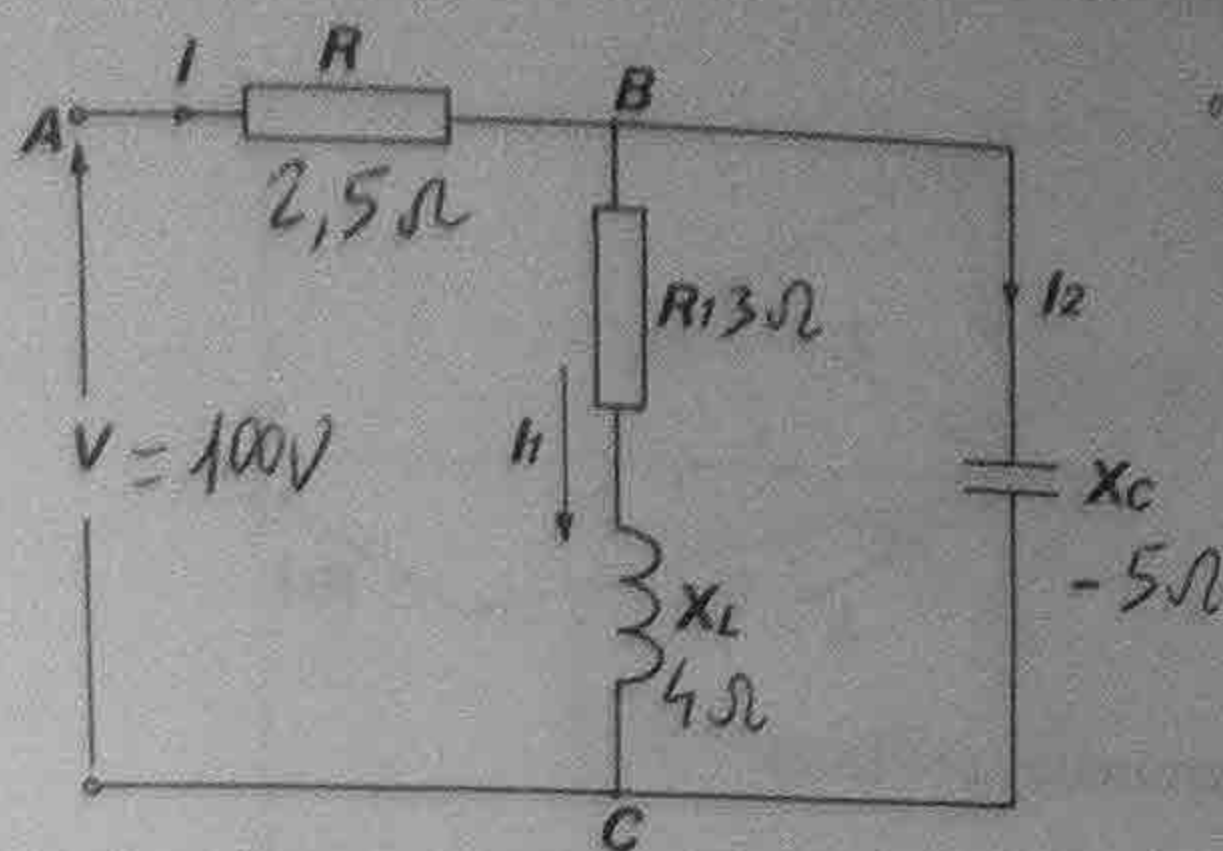


Fig. 15.26 - Circuito elettrico relativo all'esercizio 15.1.

Per la 15.73, l'impedenza totale  $Z_{AC}$  vale:

$$Z_{AC} = R + Z_{BC} = 2,5 + 7,5 - j2,5 = 10 - j2,5 (\Omega) = 10,3 \Omega \angle -14,036^\circ$$

Posto  $V$  sull'asse reale (vedi Fig. 15.27), la corrente totale  $I$  vale:

$$I = \frac{V}{Z_{AC}} = \frac{100 \angle 0^\circ}{10,3 \angle -14,036^\circ} = 9,7 \text{ A} \angle +14,036^\circ = 9,41 + j2,35 \text{ (A)}$$

Determinazione di  $I_1$  e  $I_2$ : **primo modo.**

Per determinare la  $I_1$ , basta applicare le 15.76:

$$I_1 = I \cdot \frac{-jX_C}{R_1 + jX_L - jX_C} = (9,41 + j2,35) \cdot \frac{-j5}{3 + j4 - j5} = 15,34 \text{ A} \angle -57,529^\circ = 8,24 - j12,94 \text{ (A)}$$

Analogamente:

$$I_2 = I \cdot \frac{R_1 + jX_L}{R_1 + jX_L - jX_C} = (9,41 + j2,35) \cdot \frac{3 + j4}{3 + j4 - j5} = 15,34 \text{ A} \angle 85,6^\circ = 1,18 + j15,3 \text{ (A)}$$

o, più semplicemente, per il primo principio di Kirchhoff nel nodo  $B$ :

$$I_2 = I - I_1 = 9,41 + j2,35 - (8,24 - j12,94) = 1,17 + j15,29 = 15,34 \text{ A} \angle 85,6^\circ$$

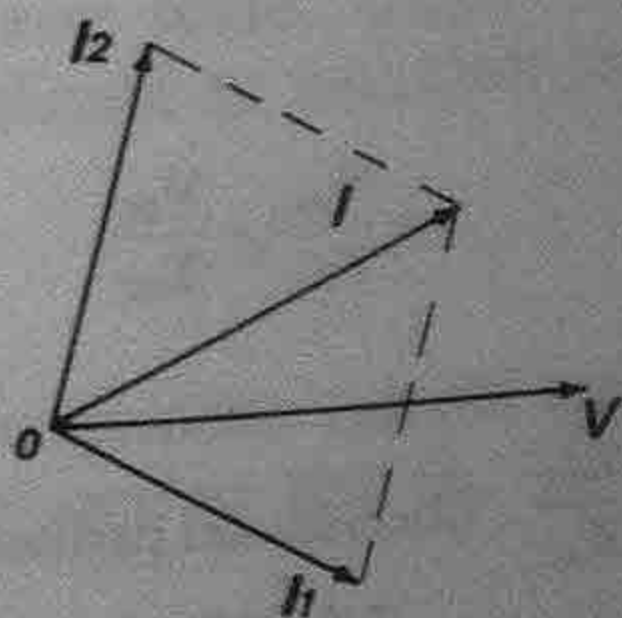


Fig. 15.27 - Diagramma vettoriale (es. 15.1).

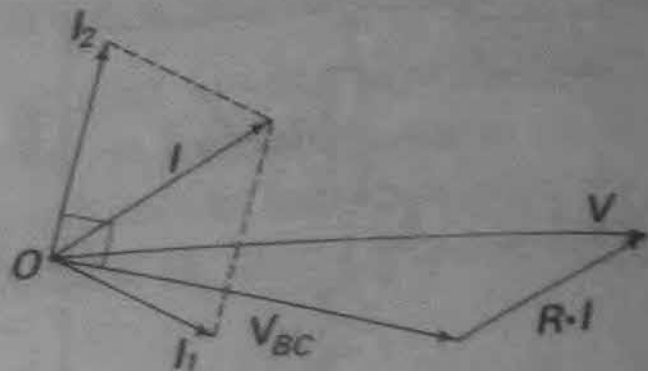


Fig. 15.28 - Diagramma vettoriale (es. 15.1).

Determinazione di  $I_1$  e  $I_2$ : secondo modo.  
Per la 9.49 si ha

$$V_{AC} = V_{AB} + V_{BC}$$

da cui (vedi Fig. 15.28):

$$\begin{aligned} V_{BC} &= V_{AC} - V_{AB} = V - R \cdot I = 100 - 2,5 \cdot (9,41 + j2,35) = \\ &= 76,475 - j5,875 \text{ (V)} = 76,7 \text{ V} \angle -4,39^\circ \text{ (2^\circ)} \end{aligned}$$

Quindi:

$$I_1 = \frac{V_{BC}}{R_1 + jX_L} = \frac{76,475 - j5,875}{3 + j4} = \frac{76,7 \angle -4,39^\circ}{5 \angle 53,13^\circ} = 15,34 \text{ A} \angle -57,52^\circ$$

$$I_2 = \frac{V_{BC}}{-jX_C} = \frac{76,7 \angle -4,39^\circ}{5 \angle -90^\circ} = 15,34 \text{ A} \angle +85,61^\circ$$